

$$4. \\ (2) \text{ 令 } \dot{I}_2 = 0$$

$$A = \frac{\dot{U}_1}{\dot{U}_2} = -1$$

$$C = \frac{\dot{I}_1}{\dot{U}_2} = 0$$

$$\text{令 } \dot{U}_2 = 0$$

$$B = \frac{\dot{U}_1}{-\dot{I}_2} = 0$$

$$D = \frac{\dot{I}_1}{-\dot{I}_2} = -1$$


$$T = \begin{bmatrix} -1 & 0 \\ 0 & -1 \end{bmatrix}$$

2.

$$\begin{aligned} H(s) &= \frac{1}{s+1} + \frac{2}{s+2} \\ &= \frac{s+2 + 2(s+1)}{(s+1)(s+2)} \\ &= \frac{3s+4}{(s+1)(s+2)} \end{aligned}$$

$$\text{令 } 3s+4=0 \quad \text{零点: } -\frac{4}{3}$$
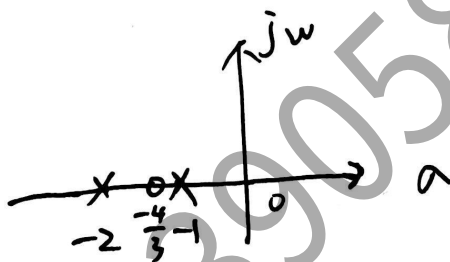
$$\text{令 } (s+1)(s+2)=0 \quad \text{极点: } -1, -2$$



1.

$$U_C(0+) = U_C(0-) = U_S =$$

$$U_C(\infty) = I_S R_2 = 2 \times 10 = 20 \text{ V}$$

$$R_0 = R_2 = 10 \Omega$$

$$\tau = R_0 C = 10 \times 0.1 \times 10^{-6} = 1 \times 10^{-6} \text{ (s)}$$

$$U_C(t) = U_C(\infty) + [U_C(0+) - U_C(\infty)] e^{-\frac{t}{\tau}}$$

$$= 20 + (U_S - 20) e^{-10^6 t} \text{ (V)} \quad (t > 0)$$

1.

$$U_C(0+) = U_C(0-) = U_S = 12V$$

$$U_C(\infty) = I_S R_2 = 2 \times 10 = 20V$$

$$R_0 = R_2 = 10\Omega$$

$$\tau = R_0 C = 10 \times 0.1 \times 10^{-6} = 1 \times 10^{-6}(s)$$


$$U_C(t) = U_C(\infty) + [U_C(0+) - U_C(\infty)] e^{-\frac{t}{\tau}}$$

~~$$= 20 + (U_S - 20) e^{-10^6 t} (V) (t \geq 0)$$~~

$$= 20 - 8e^{-10^6 t} (V) (t \geq 0)$$

5.

$$U_{C(10^-)} = 10V$$

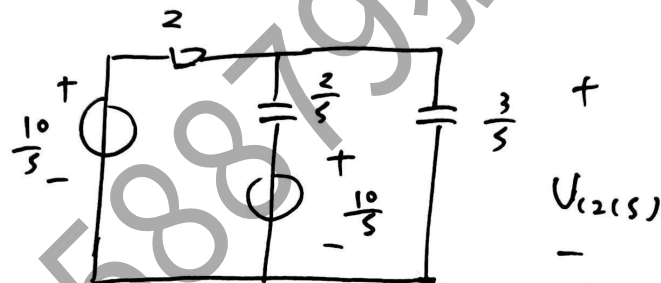

$$U_{C2(s)} = \frac{\frac{10}{s} + \frac{10}{s}}{\frac{1}{2} + \frac{s}{2} + \frac{s}{3}} = \frac{5s+5}{\frac{5}{6}s(s+\frac{3}{5})}$$

$$= \frac{10}{s} + \frac{-4}{s+0.6}$$


$$U_{C2(t)} = 10 - 4e^{-0.6t} (V)$$

2.

$$\begin{aligned}
 H(s) &= \frac{1}{s+1} + \frac{2}{s+2} \\
 &= \frac{s+2 + 2(s+1)}{(s+1)(s+2)} \\
 &= \frac{3s+4}{(s+1)(s+2)}
 \end{aligned}$$

$$\text{令 } 3s+4=0 \text{ 零点: } -\frac{4}{3}$$
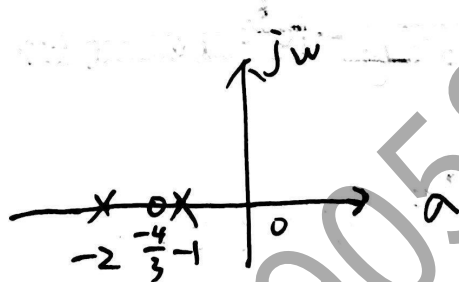
$$\text{令 } (s+1)(s+2)=0 \text{ 极点: } -1, -2$$



$$\text{设 } T = \begin{bmatrix} A & B \\ C & D \end{bmatrix}$$

4.

$$\text{令 } \dot{I}_2 = 0$$

$$A = \frac{\dot{U}_1}{\dot{U}_2} = 1$$

$$C = \frac{\dot{I}_1}{\dot{U}_2} = 0$$

$$\text{令 } \dot{U}_2 = 0$$

$$B = \frac{\dot{U}_1}{-\dot{I}_2} = 0$$

$$D = \frac{\dot{I}_1}{-\dot{I}_2} = 1$$

$$T = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix}$$

3.

$$|Z| = \sqrt{12^2 + 16^2} = 20 \Omega$$

$$\cos \varphi = \frac{12}{20} = 0.6$$

$$U_p = \frac{U_L}{\sqrt{3}} = 220 \text{ V}$$

$$I_p = \frac{U_p}{|Z|} = \frac{220}{20} = 11 \text{ A}$$

$$I_L = I_p = 11 \text{ A}$$

$$P = \sqrt{3} U_L I_L \cos \varphi$$

$$= \sqrt{3} \times 380 \times 11 \times 0.6 = 4344 \text{ W}$$

$$6. u_L = L \frac{di_L}{dt}$$

$$i_C = C \frac{du_C}{dt}$$

$$i_R = \frac{u_C}{R}$$

$$i_L = C \frac{du_C}{dt} + \frac{u_C}{R}$$

$$e(t) = L \frac{di_L}{dt} + u_C$$

$$\Rightarrow \begin{cases} \frac{du_C}{dt} = -\frac{1}{RC} u_C + \frac{1}{C} i_L \\ \frac{di_L}{dt} = -\frac{1}{L} u_C + \frac{1}{L} e(t) \end{cases}$$

$$\begin{bmatrix} \frac{du_C}{dt} \\ \frac{di_L}{dt} \end{bmatrix} = \begin{bmatrix} -\frac{1}{RC} & \frac{1}{C} \\ -\frac{1}{L} & 0 \end{bmatrix} \begin{bmatrix} u_C \\ i_L \end{bmatrix} + \begin{bmatrix} 0 \\ \frac{1}{L} \end{bmatrix} e(t)$$