
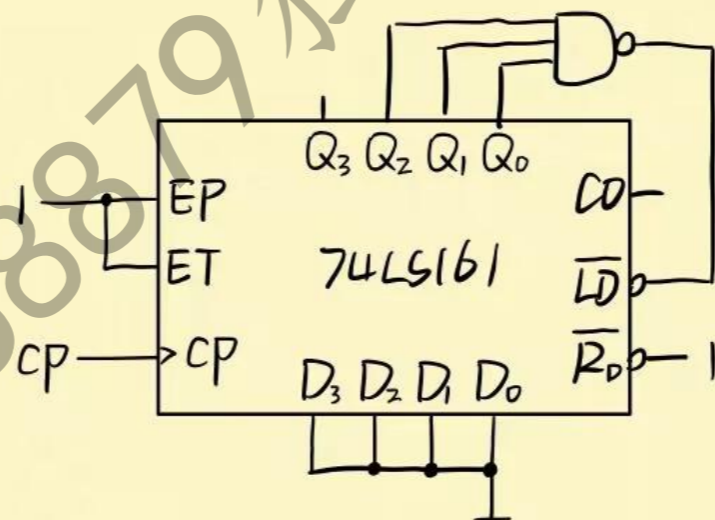


3.
采用同步置数法

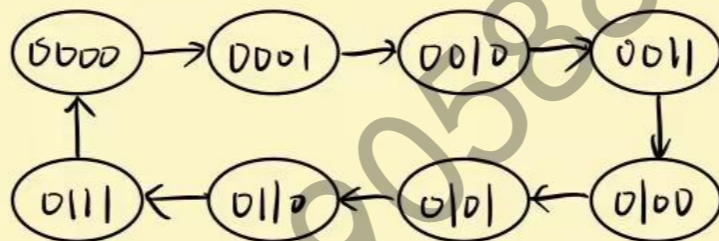


$(Q_3 Q_2 Q_1 Q_0)$




3.


采用同步置数法

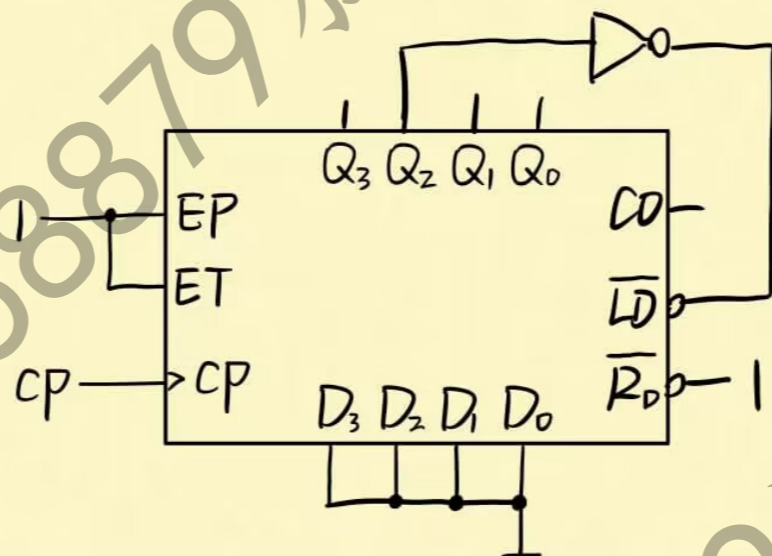

$(Q_3Q_2Q_1Q_0)$

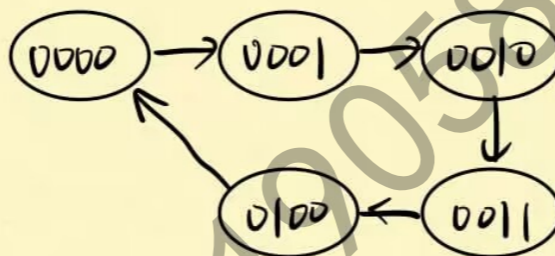

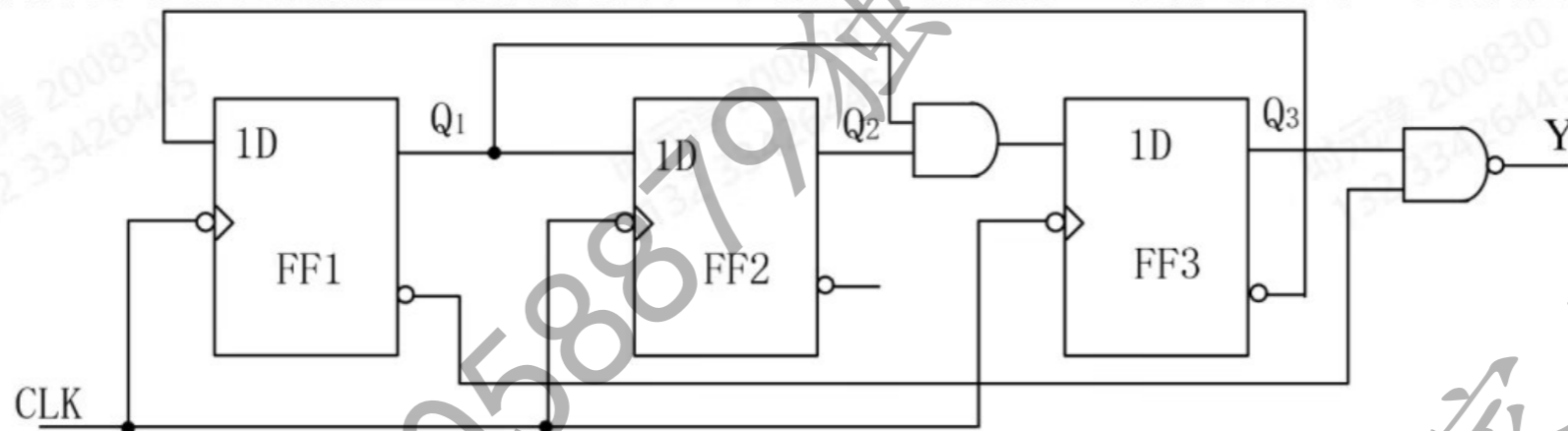2、分析图示电路的逻辑功能。写出其驱动方程、状态方程、输出方程，画出状态转换表，状态转换图，写出结论。（10分）



3、用中规模集成器件390设计一个计数器，要求计数数量与上题时序电路一致，画出接线图和状态转换图。（10分）

B I U 手机传图 Σ 代码语言 ▼


2.

$$\begin{cases} D_1 = \bar{Q}_3 \\ D_2 = Q_1 \\ D_3 = Q_2 Q_1 \end{cases}$$

$$\begin{cases} Q_1^{n+1} = \bar{Q}_3^n \\ Q_2^{n+1} = Q_1^n \\ Q_3^{n+1} = Q_2^n Q_1^n \end{cases}$$

$$Y = \overline{Q_3 Q_1} = \bar{Q}_3 + Q_1$$

Q_3^n	Q_2^n	Q_1^n	Q_3^{n+1}	Q_2^{n+1}	Q_1^{n+1}	Y
0	0	0	0	0	1	1
0	0	1	0	1	1	1
0	1	0	0	0	1	1
0	1	1	1	1	1	1
1	0	0	0	0	0	0
1	0	1	0	1	0	1
1	1	0	0	0	0	0
1	1	1	1	1	0	1

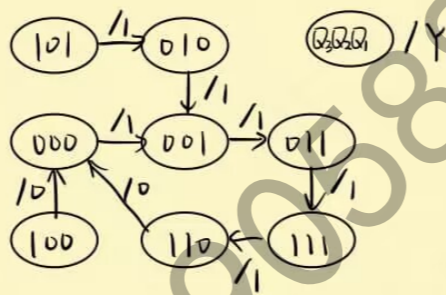

5进制计数器